

CSE 210  
Computer Architecture Sessional

Assignment-1: 4-bit ALU Simulation

Lab Section - C2  
Group - 02

15 September, 2024

Members of the Group:

- i. 2105152 - Sudip Kumar Saha
- ii. 2105161 - Sadia Naushin
- iii. 2105163 - Dibbo Chowdhury
- iv. 2105168 - Nusrat Jahan Nidhi
- v. 2105174 - Nujhat Sadia

# 1 Introduction

The Arithmetic Logic Unit (ALU) serves as the computational core of a computer's central processing unit (CPU). Responsible for executing arithmetic and logic operations, the ALU performs essential tasks such as addition, subtraction, bitwise logical operations, negation and many more. Its speed and versatility make it a vital component in processing instructions efficiently. ALUs come in various architectures, adapting to different computational demands across applications. To understand modern computing devices, knowing about the ALU – its role and design – is vital.

The ALU we designed consisted of three control signals, through which we facilitated six operations: subtraction, transfer, add with carry, increment, bitwise AND, decrement. The arithmetic unit was responsible for managing the arithmetic operations, while our logical unit executed the rest. The control signals supervised the entire ALU operations.

We also incorporated 4 status flags, Carry(C), Sign(S), Overflow(V) and Zero(Z) flags, in our design. These flags followed the rules of Assembly Language with some flexibility. They imply :

- a) **C** :- C or Carry Flag is the carry out  $C_{out}$  of the adder in the ALU. It depends on the carry output of arithmetic operations. It is reset during logical operations.
- b) **S** :- S or the Sign bit is the MSB of the output,  $O_3$ .
- c) **V** :- V is the overflow flag. This flag is only meaningful for signed numbers. If the output of an n-bit ALU exceeds the range of  $-2^{n-1}$  to  $2^{n-1} - 1$  then an overflow has occurred. V is set when the addition of two positive numbers gives negative output and vice-versa. It is always reset during logical operations.

$$\begin{aligned} O_3 &= X_3 \oplus Y_3 \oplus C_3 \\ \Rightarrow O_3 \oplus C_3 \oplus O_3 &= X_3 \oplus Y_3 \oplus C_3 \oplus C_3 \oplus O_3 \end{aligned}$$

$$C_3 = X_3 \oplus Y_3 \oplus O_3 \tag{1}$$

$$V = C_3 \oplus C_{out} \tag{2}$$

$$\therefore V = X_3 \oplus Y_3 \oplus O_3 \oplus C_{out}$$

where  $C_{out}$  is the output carry,  $O_3$  is the MSB of the output,  $X_3$  and  $Y_3$  are the MSB of the first and second input of the adder respectively.

- d) **Z** :- Z is the Zero flag, which is set when the output of the ALU is zero and reset otherwise.

$$Z = \overline{O_3 \vee O_2 \vee O_1 \vee O_0}$$

## 2 Problem Specification with Assigned Instructions

Design a 4-bit ALU with three selection bits  $cs_2$ ,  $cs_1$  and  $cs_0$  for performing the following operations:

Control Signals			Description	Function
$cs_2$	$cs_1$	$cs_0$		
X	0	0	Sub	$A + \overline{B} + 1$
X	0	1	Transfer A	$A$
0	1	0	Add with carry	$A + B + 1$
0	1	1	Increment A	$A + 1$
1	1	0	AND	$A \wedge B$
1	1	1	Decrement A	$A - 1$

Table 1: Problem Specification

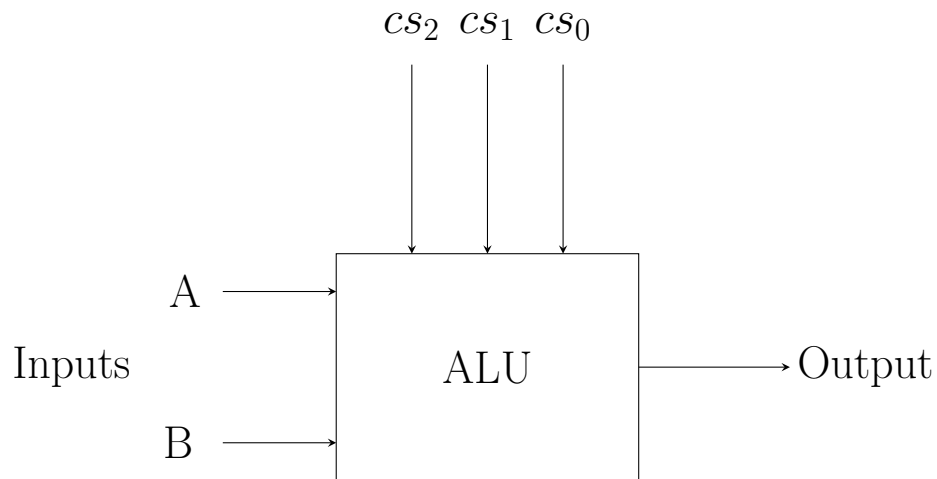


Figure 1: 4-bit ALU

### 3 Detailed Design Steps with K-maps

#### 3.1 Design Steps

- i) Our design comprises 4 parts: arithmetic unit, logical unit, selection control, and status flags.
- ii) The arithmetic unit computes 5 arithmetic operations (subtract, transfer A, add with carry, increment A, decrement A) with the help of a 4-bit parallel adder, basic gates and two multiplexer.
- iii) Here we have modified the input into the adder in such a way so that we don't need to modify the output after getting the output from adder.
- iv) From the truth table 3, we see that the  $X_i$  can be either  $A$  or  $A \wedge B$ . MUX:3 is just doing that.
- v) For  $Y_i$  as there are four possible values, we constructed another truth table with two **Intermediate Selection Bits** namely  $S_1, S_2$  in Table 2. And as we are using 2 to 1 MUX for MUX:3, so we stuck with 2 to 1 MUX for the rest of the design. Using 4 to 1 MUX would not have lessened the amount of ICs.

$S_2$	$S_1$	$Y_i$
0	0	0
0	1	1
1	0	$B$
1	1	$\overline{B}$

Table 2: Determining  $Y_i$

- vi) Now the logical unit is comprised of a 4-bit 2X1 multiplexer with  $S_0$  selection bit. Logical operation  $AB$  is selected when  $S_0$  is 1 and  $A$  is selected when  $S_0$  is 0. The only logical operation occurs when the combination of  $C_{S2}, C_{S1}$  and  $C_{S0}$  is 110. So the value of  $S_0$  will be 1 when  $S_0 = C_{S2}C_{S1}\overline{C_{S0}}$
- vii) For calculating the flags, we used the formula described in section:1.

### 3.2 Truth Table

$C_{S2}$	$C_{S1}$	$C_{S0}$	$X_i$	$Y_i$	$Z$	$S_2$	$S_1$	$S_3$	Output
X	0	0	$A_i$	$\overline{B_i}$	1	1	1	0	$A - B$
X	0	1	$A_i$	0	0	0	0	0	A
0	1	0	$A_i$	$B_i$	1	1	0	0	$A + B + 1$
0	1	1	$A_i$	0	1	0	0	0	$A + 1$
1	1	0	$A_i B_i$	0	0	0	0	1	AB
1	1	1	$A_i$	1	0	0	1	0	$A - 1$

Table 3: Truth Table for  $S_1$ ,  $S_2$  selection bits and carry input of the adder

### 3.3 K-maps

#### 3.3.1 K-map for $S_1$

$S_1$  is the selection bit with input  $B$  and  $\overline{B}$  and it's output goes to the multiplexer with  $S_2$

$C_{S1}, C_{S0}$		00	01	11	10
		$C_{S2}$			
0		1	0	0	0
1		1	0	1	0

From the K-map:  $S_1 = \overline{C_{S1}} \overline{C_{S0}} + C_{S2} C_{S1} C_{S0}$

#### 3.3.2 K-map for $S_2$

$S_2$  is the selection bit with the inputs:  $S_1$ , Output of  $S_1$ . The output of this multiplexer determines  $Y_i$ .

$C_{S1}, C_{S0}$		00	01	11	10
		$C_{S2}$			
0		1	0	0	1
1		1	0	0	0

From the K-map:  $S_2 = \overline{C_{S1}} \overline{C_{S0}} + \overline{C_{S2}} \overline{C_{S0}}$

### 3.3.3 K-map for $Z$

$Z$  is the carry input of our adder.

$C_{S1}, C_{S0}$					
		00	01	11	10
$C_{S2}$	0	1	0	1	1
	1	1	0	0	0

From the K-map:  $Z = \overline{C_{S1}} \overline{C_{S0}} + \overline{C_{S2}} C_{S1}$

## 4 Block Diagram

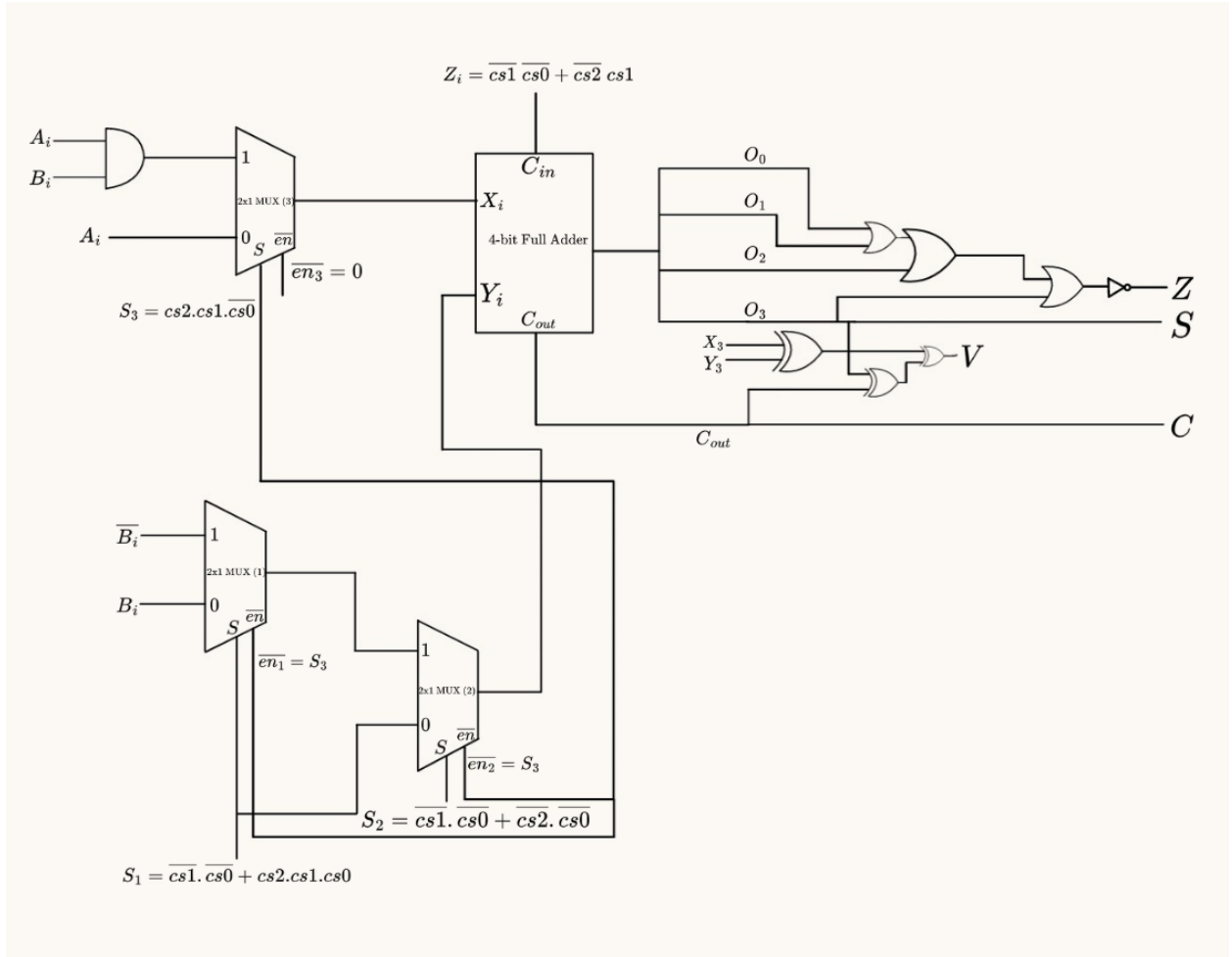


Figure 2: Block Diagram of ALU

## 5 Complete Circuit diagram

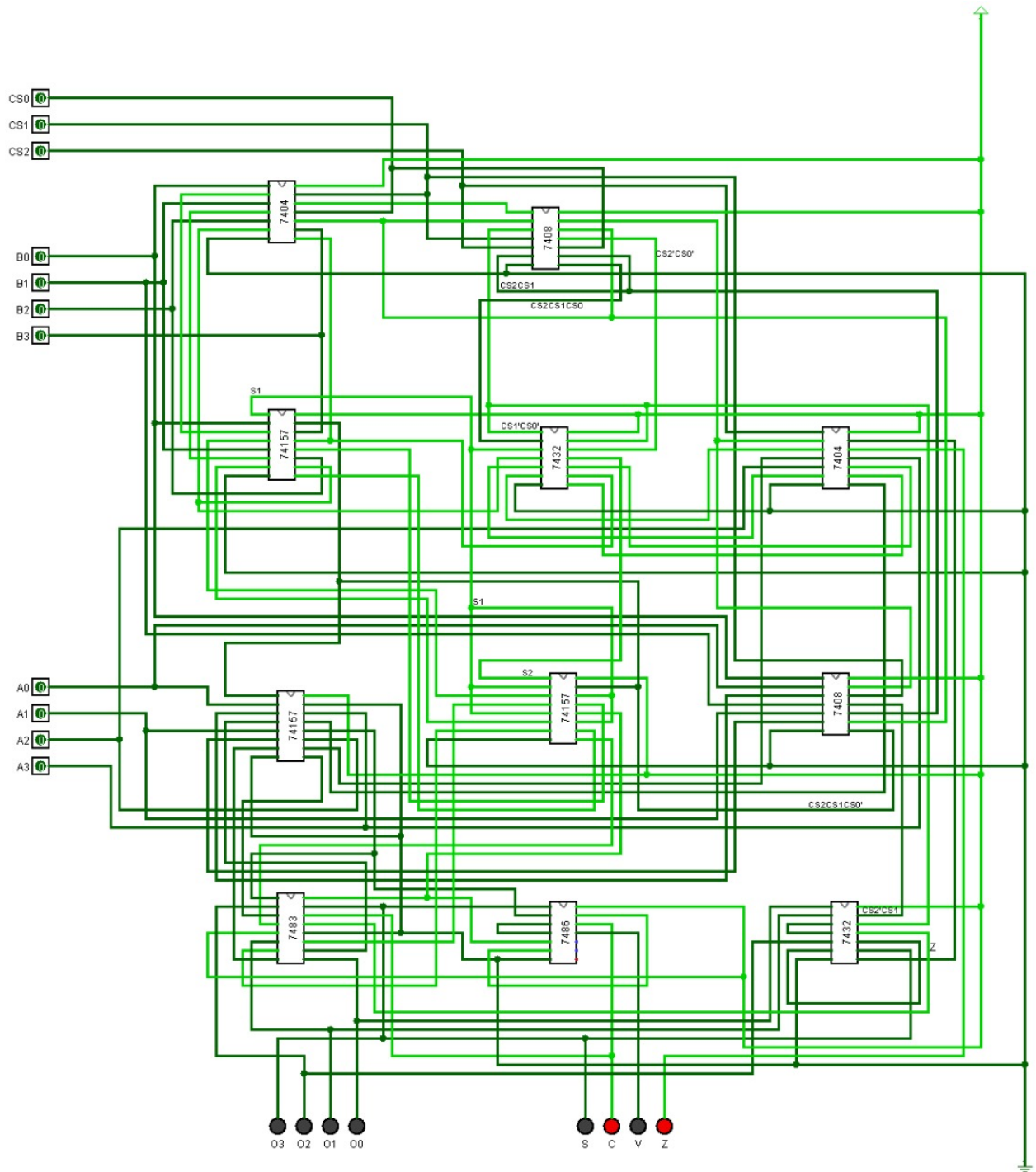


Figure 3: Complete ALU circuit

## 6 TinkerCAD Design

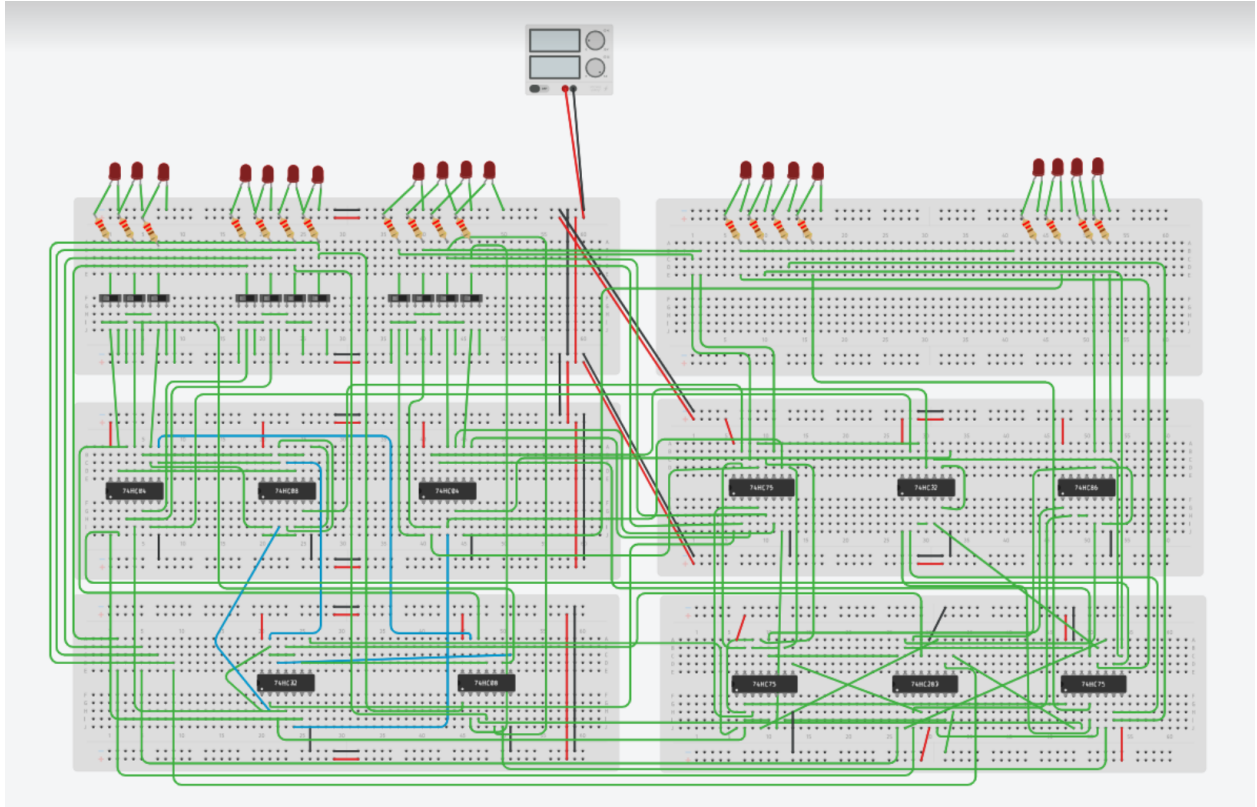


Figure 4: TinkerCAD design for hardware implementation

## 7 ICs used with count as a chart

IC	Number of ICs
7483	1
74157	3
7432	2
7486	1
7404	2
7408	2
Total	11

Table 4: ICs and their number



## 8 The Simulator Used along with the Version Number

Logisim - generic - 2.7.1

## 9 Discussions

In this 4-bit ALU design, we have efficiently combined both arithmetic and logical operations using basic gates, multiplexers, and a parallel adder.

We started off by making the truth table and finding equations. But in this traditional way in which we tried to find the values of  $X_i$  and  $Y_i$  separately, we got huge equations and led to extensive use of ICs. So we had to optimize the situation by using MUX. We narrowed the number of ICs down to 11.

Some difficulties did arise while software simulation using **Logisim**. Changes had to be made in the 7400-lib.circ. The  $C_{out}$  pin of the IC7483 in the library was faulty. This problem was corrected using a separate IC7483.circ file in our final ALU software simulation.

Finally, we addressed challenges in the hardware implementation by correcting issues with LEDs, where the use of different types initially caused a power drop. Overheating problems due to connecting LEDs without resistances were resolved through the implementation of proper corrections. The challenge of maintaining a stable power flow across six breadboards was successfully addressed through multiple correction attempts. The flags are calculated based on the output and control signals, ensuring accurate status reporting for operations. This design approach balances functionality and simplicity, providing a solution for basic arithmetic and logic tasks in a compact 4-bit system.

## 10 Contribution of Each Member

- 2105152 : Sudip Kumar Saha
  - Logisim circuit design
  - Software simulation of ALU circuit
  - Hardware
  - Report writing
- 2105161 - Sadia Naushin
  - Software simulation of ALU circuit
  - Hardware
  - Report writing

- 2105163 - Dibbo Chowdhury
  - Circuit design and optimization
  - TinkerCAD design
  - Hardware
  - Report writing
- 2105168 - Nusrat Jahan Nidhi
  - Hardware
  - Report writing
- 2105174 - Nujhat Sadia
  - Circuit design and optimization
  - Software simulation of ALU circuit
  - Hardware implementation
  - Report writing